 


# CSE 331 HW2 REPORT

Firstly, since using xor gate is prohibited, created a xor module.

By using this diagram I created my xor module. I used 2 NOT gate and 2 AND gate and also to fetch result I “OR”ed results of AND.



This is testbench results of XOR.


```
VSIM19> run -all
# A: 0 B: 0 and Result: 0
# A: 1 B: 0 and Result: 1
# A: 0 B: 1 and Result: 1
# A: 1 B: 1 and Result: 0
# ** Note: $Finish      : /home/Euckan/Desktop/161044001/my_xor_bench.v(15)
#    Time: 400 ps  Iteration: 0  Instance: /my_xor_bench
# 1
# Break in Module my_xor_bench at /home/Euckan/Desktop/161044001/my_xor_bench.v line 15
```

After creating XOR module, Project ready to go next phases.

To create 4x1 MUX I used block diagram.

As shown in diagram, I used 2 NOT gate to invert select bits. After that to obtain selected values, I used 4 AND gate and finally to get final result I used and or gate.

 At testbench, I changed test bench step by step and I also changed Inputs to select always 1. As shown in output, mux selected always 1 but at last case I changed select bit to any one of the 0's and as a result, I get 0 as expected.



This is my testbench result for 4x1 MUX.


```
VSIM19> run -all
# Select Bits: 00 and Result: 1
# Select Bits: 01 and Result: 1
# Select Bits: 10 and Result: 1
# Select Bits: 11 and Result: 1
# Select Bits: 10 and Result: 0
# ** Note: $Finish      : /home/Euckan/Desktop/161044001/mux_4x1_bench.v(34)
#    Time: 500 ps  Iteration: 0  Instance: /mux_4x1_bench
# 1
```



Before creating 32-bit ALU we must consider that 0 to 31 bit, 31 bit ALU must be different than others. This is a special case for MSB bit and determines some values of overall result. This ALU performs all operations that performed on 1-bit ALU but at end we must determine that is there any overflow, and also according to subtraction and overflow result, we must determine less input of 0<sup>th</sup> bit of 32-bit ALU. This can be done for overflow by performing XOR between last Carry Input and last Carry Output. For set-on-less-than input of 0<sup>th</sup> bit, we again perform XOR between overflow and subtraction result. Result of last XOR connected to 0<sup>th</sup> bit less input.

For MSB ALU adding these two line to normal 1-bit ALU is sufficient.
 
```
my_xor v_xor(V, Cin, Cout);
my_xor set_xor(set, V, fourth_and);
```



For 32-bit ALU we use 31 1-bit ALU and 1-bit MSB ALU. We give Carry Output of one ALU to next ALU Carry Input. We do operations one by one, step by step and calculation result from LSB to MSB. At the end we determine less value and also is there any overflow. At first all less inputs will be 0 but at the end we determine less result is 0 or 1 by looking its set value. At last bit we must use MSB ALU for finding these results. For 30 1-bit ALU we have 30 XOR module, which has 60 NOT gate 60 AND gate and 30 OR gate. And 30x3 OR gate for 1-bit ALU, 30x4 AND gate and also 30x2 NOT gate. For MSB-bit ALU we have 3 OR gate, 4 AND gate, 2 NOT gate and additionally one xor module for Overflow flag and one xor module for set value. Also to determine which operation occurring currently, we have 32 4x1MUX.

At the end for 32-bit we have 324 AND gate, 162 OR gate, 196 NOT gate for 32-bit ALU.

TEST RESULTS IN NEXT PAGE.

This is test result of 32-bit ALU desing.

```
V$IM 12> cua -all
# OPCODE: 000
# A: 10101010101010101010101010101010
# B: 01010101010101010101010101010101
# Result: 00000000000000000000000000000000, Cout: 0 V: 0
# OPCODE: 000
# A: 00000000000000001111111111111111
# B: 11111111111111110000000000000000
# Result: 00000000000000000000000000000000, Cout: 0 V: 0
# OPCODE: 001
# A: 10101010101010101010101010101010
# B: 01010101010101010101010101010101
# Result: 11111111111111111111111111111111, Cout: 0 V: 0
# OPCODE: 001
# A: 00000000000000001111111111111111
# B: 11111111111111110000000000000000
# Result: 11111111111111111111111111111111, Cout: 0 V: 0
# OPCODE: 010
# A: 10101010101010101010101010101010
# B: 01010101010101010101010101010101
# Result: 11111111111111111111111111111111, Cout: 0 V: 0
# OPCODE: 010
# A: 00000000000000001111111111111111
# B: 11111111111111110000000000000000
# Result: 11111111111111111111111111111111, Cout: 0 V: 0
# OPCODE: 110
# A: 10101010101010101010101010101010
# B: 01010101010101010101010101010101
# Result: 01010101010101010101010101010101, Cout: 1 V: 1
# OPCODE: 110
# A: 00000000000000001111111111111111
# B: 11111111111111110000000000000000
# Result: 00000000000000001111111111111111, Cout: 0 V: 0
# OPCODE: 111
# A: 10101010101010101010101010101010
# B: 01010101010101010101010101010101
# Result: 00000000000000000000000000000001, Cout: 1 V: 1
# OPCODE: 111
# A: 00000000000000001111111111111111
# B: 00000000000000000000000000000001
# Result: 00000000000000000000000000000000, Cout: 1 V: 0
# ** Note: 5faish : /home/Euckan/Desktop/161044001/thicty_two_bit_alu_bench.v(49)
# Time: 1200 ps Iteration: 0 Instance: /thicty_two_bit_alu_bench
# 1
```